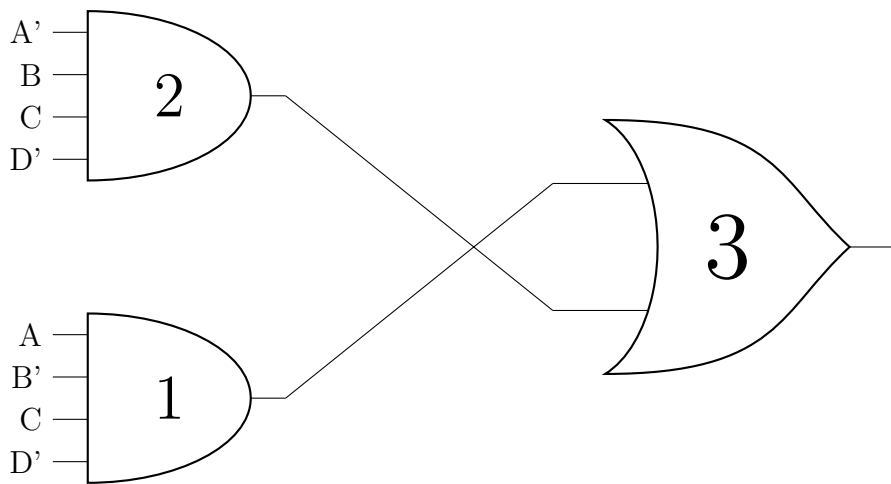


Logic Gate Representation 2.5B

Yugal Garg

December 31, 2020



$$b = AB'CD' + A'BCD' \quad (2.5)$$